

# I-CHIP PS 1

Done by Ashutosh Awasthi and Neeraj Kumar

March 21, 2023

## 1 EXPLANATION OF CALC MODULE

The Input and Output variables are taken exactly as mentioned in PS. We have implemented DataFlow Modelling to solve the PS. Our logic behind is that if  $zx$  is 0, wire  $x1$  is given value of  $x$  and otherwise 0. Now if  $nx$  is 0, wire  $x2$  is given value of  $x1$  and otherwise  $!x1$  (means inverting each bit). Similarly values of  $y1$  and  $y2$  are obtained based on values of  $zy$  and  $ny$ . Then on basis of value of ' $f$ ' is 1 or 0, wire  $z1$  is assigned a value  $(x2+y2)$  or  $(x2\&y2)$ , respectively. Output variable ' $o$ ' is given value  $z1$  if ' $no$ ' is 0 and otherwise  $!z1$ . Output variable ' $zr$ ' is given value as negation of ' $o$ ' (unary operator which performs OR operation on all bits) because if OR of all the bits of ' $o$ ' is zero then  $o$  is zero, that means  $zr$  will be 1. As output ' $o$ ' is a signed number the 7th bit i.e, MSB will give the sign of the number. Therefore  $o[7]$  is equal to  $ng$ .

## 2 CONTROL BITS FOR DESIRED OUTPUTS

Desired Output	$zx$	$nx$	$zy$	$ny$	$f$	$no$
0	1	0	1	0	0	0
1	1	1	1	1	1	1
-1	1	1	1	0	1	0
$x$	0	0	1	0	1	0
$y$	1	0	0	0	1	0
$!x$	0	1	1	0	1	0
$!y$	1	0	0	1	1	0
$-x$	0	0	1	1	1	1
$-y$	1	1	0	0	1	1
$x+1$	0	1	1	1	1	1
$y+1$	1	1	0	1	1	1
$x-1$	0	0	1	1	1	0
$y-1$	1	1	0	0	1	0
$x+y$	0	0	0	0	1	0
$x-y$	0	1	0	0	1	1
$y-x$	0	0	0	1	1	1
$x\&y$	0	0	0	0	0	0
$x y$	0	1	0	1	0	1